

# Group 5 lab 1 report

Ashley Björs, Elliot Bodin, Daniel Rytenberg, Jonas Gerne

January 2024

## 1 LUT list

```
Report Cell Usage:
+-----+-----+-----+
|      |Cell |Count |
+-----+-----+-----+
|1      |LUT2 |      1|
|2      |IBUF |      2|
|3      |OBUF |      1|
+-----+-----+-----+
```

Figure 1: This is the LUT list of step 1

```
Report Cell Usage:
+-----+-----+-----+
|      |Cell |Count |
+-----+-----+-----+
|1      |LUT3 |      1|
|2      |IBUF |      3|
|3      |OBUF |      1|
+-----+-----+-----+
```

Figure 2: This is the LUT list of step 2

```

Report Cell Usage:
+-----+-----+-----+
|      |Cell |Count |
+-----+-----+-----+
|1      |LUT6 |      1|
|2      |IBUF |      6|
|3      |OBUF |      1|
+-----+-----+-----+

```

Figure 3: This is the LUT list of step 3

```

Report Cell Usage:
+-----+-----+-----+
|      |Cell |Count |
+-----+-----+-----+
|1      |LUT6 |      1|
|2      |IBUF |      6|
|3      |OBUF |      1|
+-----+-----+-----+

```

Figure 4: This is the LUT list of step 4

```

Report Cell Usage:
+-----+-----+-----+
|      |Cell |Count |
+-----+-----+-----+
|1      |IBUF |      1|
|2      |OBUF |      2|
+-----+-----+-----+

```

Figure 5: This is the LUT list of step 5

## 2 Simulations

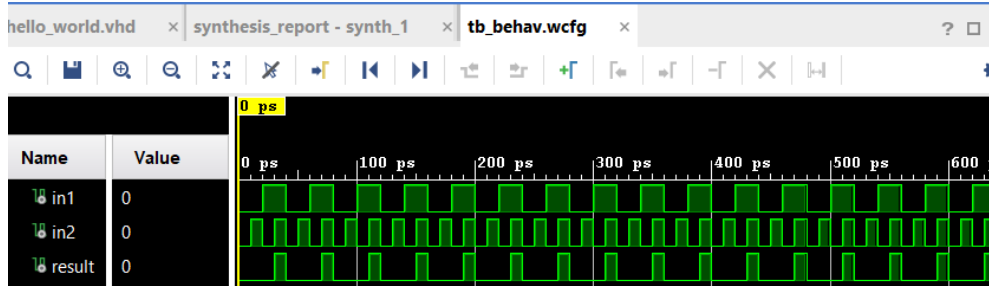


Figure 6: This is the simulation of step 1

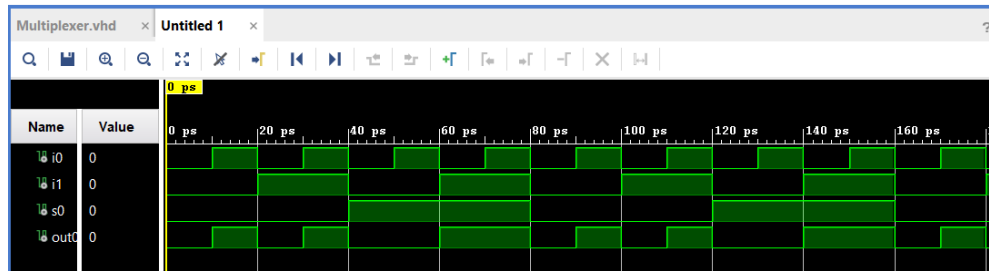


Figure 7: This is the simulation of step 2

The following components are 3 different ways to implement an 4 to one bit mux. The IO are the following:

- i0-i3 are inputs.
- s0,s1 are select for the following input values.
- out0 are the output from the 4 to 1 mux.

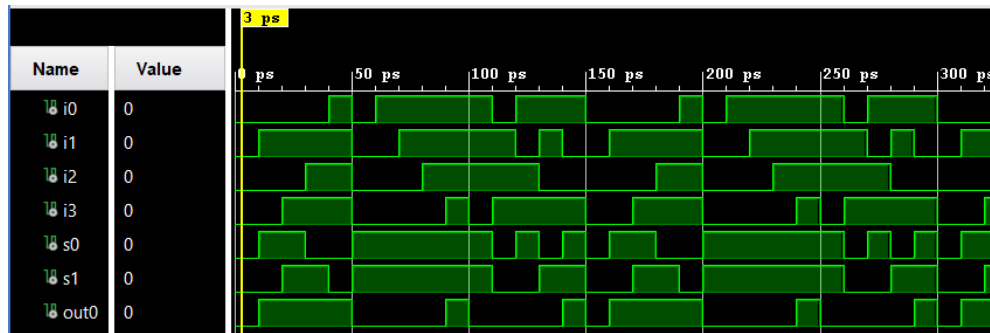


Figure 8: This is the simulation of step 3

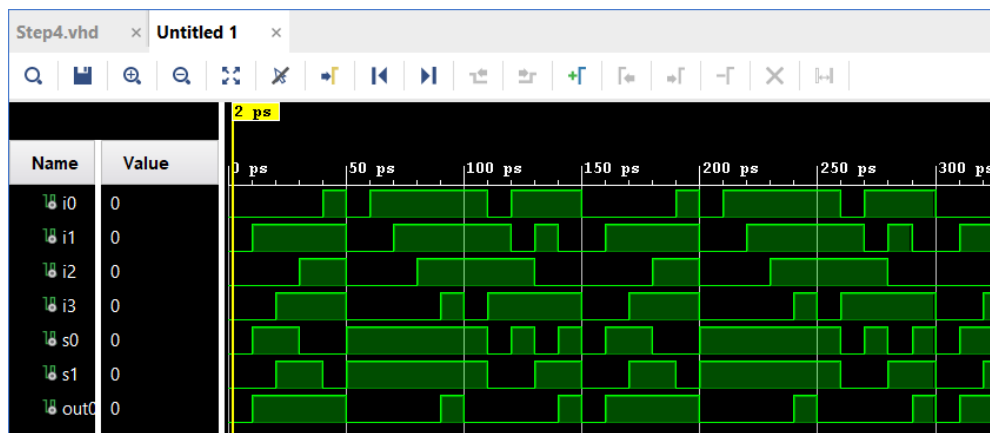


Figure 9: This is the simulation of step 4

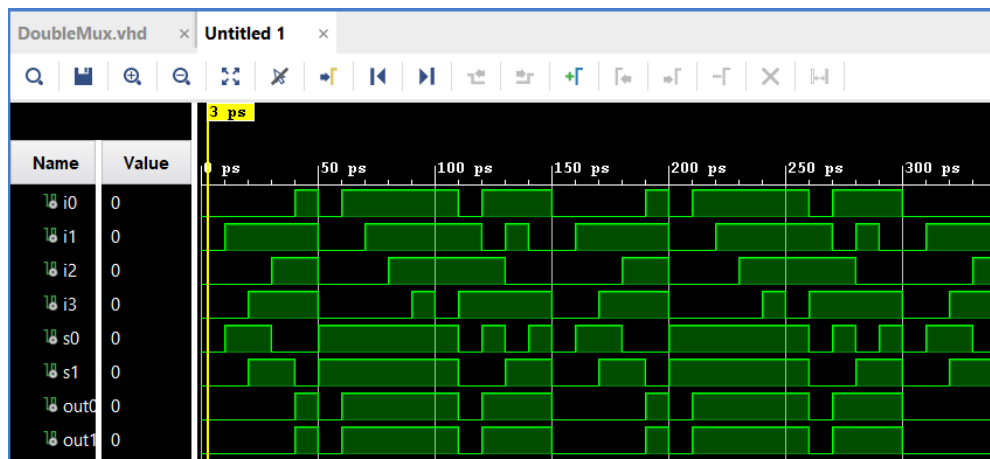


Figure 10: This is the simulation of step 5